



CMSC 11: Introduction to Computer Science

Jaderick P. Pabico <jppabico@uplb.edu.ph>
Institute of Computer Science, CAS, UPLB

Review



- Flip-flop in action : how flip-flop remembers the previous output

S	R	Q	Not-Q
1	1	No change	
1	0	0	1
0	1	1	0
0	0	Disallowed	



Flip-flop trivia


- Flip-flop is also called a LATCH
- Because it “locks in” data





Registers

 - If the flip-flop is a device for storing one bit, a REGISTER stores several bits simultaneously
- It's like a row of boxes, each holding one bit



- Does a row of flip-flops do the job?


Well, sort of!

BUT, if you try and make this work by hooking up some inputs to R-S flip-flops, you may find yourself growing confused!




Registers

 - The solution is to add a GATING NETWORK to the basic R-S flip-flop:




- D = data, E= enable
- The GATING NETWORK does not allow the DISALLOWED state for the flip-flop

Registers

 

- When $E=1$, then $R=D$ and $S=\text{Not}D$.
- Hence, the value of D is stored at Q
- IOW, $E=1$ ENABLES the bit D to be loaded into the flip-flop

Registers

 

- When $E=0$, then S and R both become 1,
- and the flip-flop does not change
- IOW, $E=0$ BLOCKS the arrival of more data.



Boxes in a box

- Computers are black boxes made of boxes that are made of boxes that are made of boxes...




Gated Flip-Flop



- So, in the spirit of ignoring the inner workings once they are understood...

 
Or even without understanding them...
- We incorporate the GATING NETWORK into the box and draw the GATED FLIP-FLOP like so:





Parallel Register

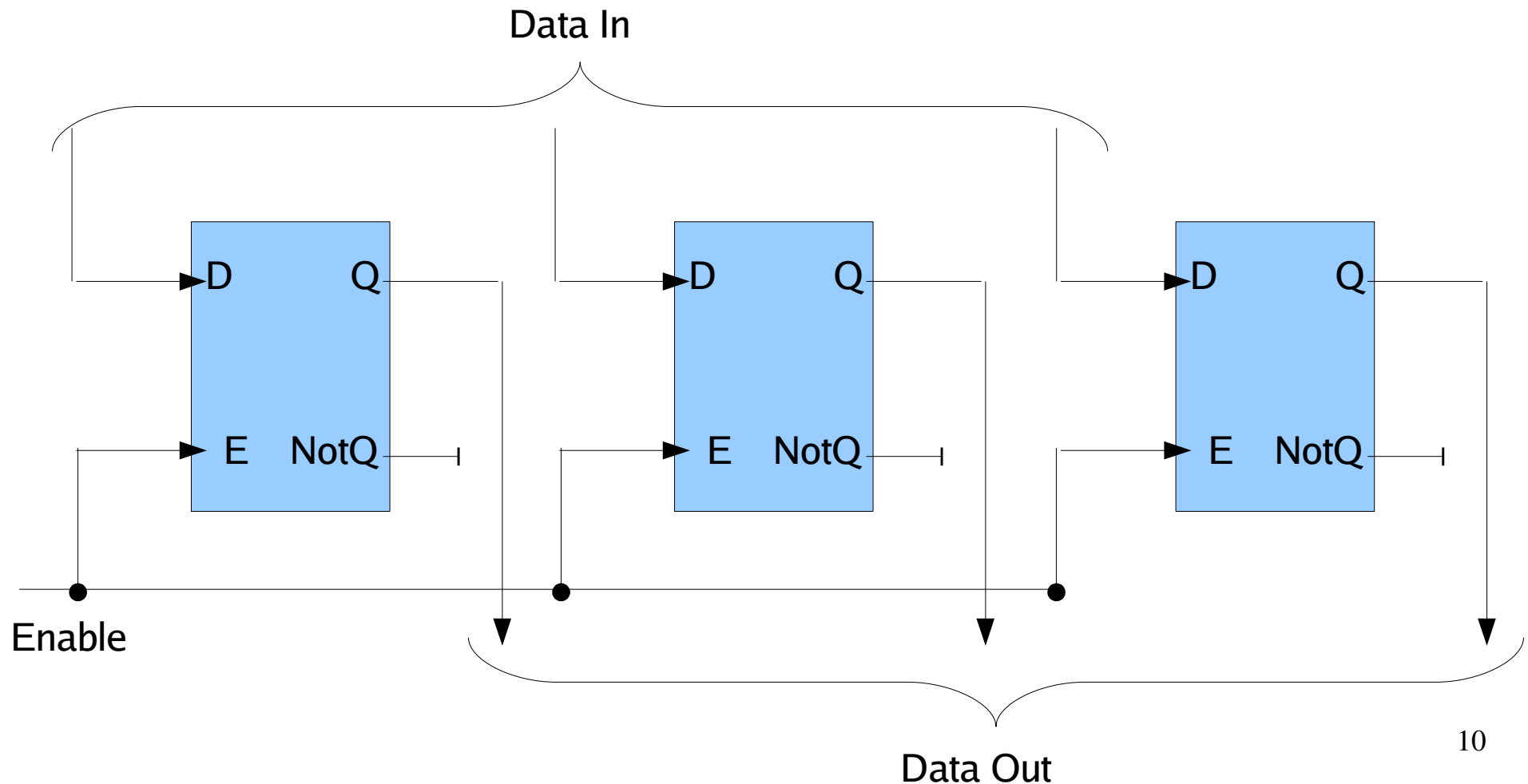
- Then here is a parallel register that stores 3 bits





Parallel Register

 - On $E=1$, 3 bits are simultaneously loaded into the register



- Now, what controls the ENABLE input?

TIME



We are a basic fact of
computer life!

Computers won't be
computers without us,
bwa, ha, ha, ha, ha!



TIME



- As soon as you begin storing data, questions of TIMING arise:
 - How long do you store data?
 - When do you move data?
 - How do you synchronize signals?
- These issues are so critical that logic with memory is called SEQUENTIAL LOGIC
- Thus, to keep sequential logic in step:
ALL COMPUTERS HAVE CLOCKS




We are
the
necessary
evils!

TIME




 
- The clock's pulse is the computer's heartbeat
- Only, instead of a warm, ragged human heartbeat, like this:




TIME



  - The computer's pulse is square and cold:



TIME

 


- One clock pulse is the burst of electrical current when clock output = 1
- One cycle is the interval from the beginning of a pulse to the beginning of the next.

TIME



 - Depending on the computer, the clock frequency may be hundreds of thousands to billions of cycles per second




TIME



- The idea of using a clock is that the computer's logical state should change **ONLY** on the clock pulse.
- Ideally, when the clock hits 1, all signals move, then stop on clock=0


Then go... then stop... then go...

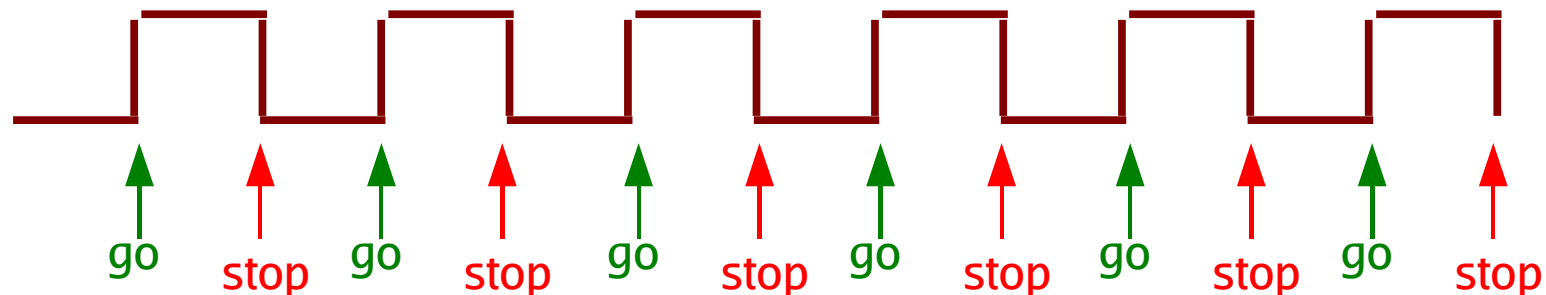

TIME



 - A typical example is to attach the clock to the ENABLE input of the gated flip-flop
- in which case the flip-flop becomes known as the D Flip-Flop
- Then a new bit of data is loaded at every clock pulse



TIME



- Unfortunately, things are rarely ideal
- It takes a non-zero time for a signal to pass along a wire
- so things are never perfectly synchronized

This is what is called as
PROPAGATION DELAY


Yeah, electrons pass
through wires at nearly
 C

And C is the
speed of light in
vacuum!

TIME




 - For example, suppose at an AND-gate, one input is changing from 1 to 0, and the other from 0 to 1.




- If A and B did not change at the same time,
- Say A changes after B, the output will have an unwanted pulse.


TIME

 


CLOCK

 


A

 

B

 

OUTPUT

 

- This pulse is a GLITCH
- And brief as it is, it can cause a flip-flop to flop!

Next Meeting



- Memory

